

Phsx 2220 - Homework #8


- 32-1. The magnetic field of Earth can be approximated as the magnetic field of a dipole, with horizontal and vertical components, at a point a distance r from Earth's center, given by

$$B_h = \frac{\mu_0 \mu}{4\pi r^3} \cos \lambda_m, \quad B_v = \frac{\mu_0 \mu}{2\pi r^3} \sin \lambda_m,$$


where λ_m is the magnetic latitude (latitude measured from the geomagnetic equator toward the north or south geomagnetic pole.) Assume that Earth's magnetic dipole moment is $\mu = 8.00 \times 10^{22} \text{ A}\cdot\text{m}^2$. Find the magnitude and inclination of Earth's magnetic field (the angle the magnetic field makes with the horizontal) at (a) the geomagnetic equator; (b) a point at geomagnetic latitude 60° ; (c) the north geomagnetic pole.

- 32-2. Measurements in mines and boreholes indicate that Earth's interior temperature increases with depth at the average rate of $30^\circ\text{C}/\text{km}$. Assuming a surface temperature of 10°C , at what depth does iron cease to be ferromagnetic? (The Curie temperature of iron varies very little with pressure.)
- 32-3. The induced magnetic field 6.0 mm from the central axis of a circular parallel-plate capacitor and between the plates is $2.0 \times 10^{-7} \text{ T}$. The plates have radius 3.0 mm. At what rate dE/dt is the electric field between the plates changing?
- 32-4. At what rate must the potential difference between the plates of a parallel-plate capacitor with a $2.0 \mu\text{F}$ capacitance be changed to produce a displacement current of 1.5 A ?

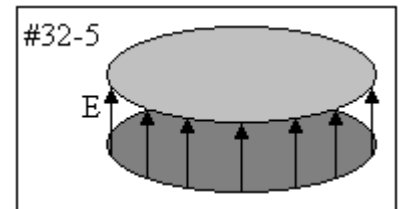
- 32-5. The magnitude of the electric field between the two circular plates of the parallel-plate capacitor shown at right is $E = (4.0 \times 10^5) - (6.0 \times 10^4 t)$, with E in volts per meter and t in seconds. At $t = 0$, the field is upward as shown. The plate area is $4.0 \times 10^{-2} \text{ m}^2$. For $t \geq 0$, (a) what are the magnitude and direction of the displacement current between the plates and (b) is the direction of the induced magnetic field clockwise or counter-clockwise around the plates?



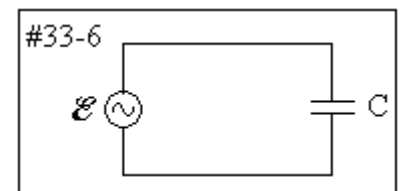- 33-6. A $1.5 \mu\text{F}$ capacitor is connected as shown at right to an ac generator with $\mathcal{E}_m = 30.0 \text{ V}$. What is the amplitude of the resulting alternating current if the frequency of the emf is (a) 1.00 kHz and (b) 8.00 kHz ?



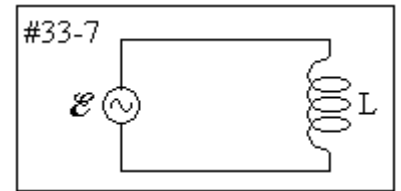- 33-7. A 50.0 mH inductor is connected as shown at right to an ac generator with $\mathcal{E}_m = 30.0$ V. What is the amplitude of the resulting alternating current if the frequency of the emf is (a) 1.00 kHz and (b) 8.00 kHz?



- 33-8. Can the amplitude of the voltage across an inductor be greater than the amplitude of the generator emf in an RLC circuit? Consider an RLC circuit with $\mathcal{E}_m = 10$ V, $R = 10 \Omega$, $L = 1.0$ H, and $C = 1.0 \mu\text{F}$. Find the amplitude of the voltage across the inductor at resonance.
- 33-9. A coil of inductance 88 mH and an unknown resistance and a $0.94 \mu\text{F}$ capacitor are connected in series with an alternating emf of frequency 930 Hz. If the phase constant between the applied voltage and the current is 75° , what is the resistance of the coil?
- 33-10. An air conditioner connected to a 120 V rms ac line is equivalent to a 12.0Ω resistance and a 1.30Ω inductive reactance in series. (a) Calculate the impedance of the air conditioner. (b) Find the average rate at which power is supplied to the appliance.
- 33-11. An electric motor has an effective resistance of 32.0Ω and an inductive reactance of 45.0Ω when working under load. The rms voltage across the alternating source is 420 V. Calculate the rms current.
- 33-12. A generator supplies 100 V to the primary coil of a transformer of 50 turns. If the secondary coil has 500 turns, what is the secondary voltage?