- For the circuit shown at right, how much charge is on capacitor C₂?
- 2. What is the area of each plate of a 1 μF capacitor if the plates are separated by 1 mm?
- 3. If the capacitor in the previous problem is attached to a 12 V battery, what is the magnitude of the electric field between the plates?
- Find the charge on each capacitor, and the voltage across each capacitor, in the circuit shown.
- 5. Find the energy stored in each capacitor in the previous problem.
- 6. When a 2 Ω load resistor is attached to a battery with an emf of 12 V, the power dissipated by the load resistor is 50 W. What is the internal resistance of the battery?
- 7. A 15 V battery has an internal resistance of 0.5 Ω (shown below the battery). What is the current i?
- 8. What is the voltage across the 4 Ω resistor in problem 7?
- 9. What is the power dissipated by the 3 Ω resistor in problem 7?
- 10. A current of 2 A flows through the 4.5 Ω resistor. Find the voltage between points a and b.
- 11. Write down three Kirchhoff's rules that are sufficient to solve the circuit shown.



 $\mathcal{E} = 12V$ $\downarrow + C_1 = 2\mu F$



- 12. An RC circuit with R = 2 x $10^4 \Omega$ and C = 5 μ F is charged with a 30 V battery. What is the time constant of the circuit?
- 13. In problem 12, find the time for the capacitor to reach 1/4 of its final charge Q, and find the final charge Q on the capacitor.



C3=111



- 14. In problem 12, find the initial current at t = 0, and find the current at t = 0.1 s.
- 15. A proton with $v = 3 \times 10^6$ m/s enters a magnetic field of 1.8 T at a 30° angle. What is the force on the proton?
- 16. A proton moves perpendicular to a magnetic field of 0.005 T. What is the period of the proton's circular orbit?
- 17. An electron with $v = 4.47 \times 10^5$ m/s moves perpendicular to a magnetic field 5 x 10^{-5} T, as shown. What is the acceleration of the electron? What is the radius of the electron's orbit?
- 18. A horizontal wire 70 m long carries a current of 30 A. If the Earth's magnetic field is 5 x 10^{-5} T as shown, find the magnetic force on the wire.
- 19. A wire is bent in the shape of 3/4 of a circle of radius 15 cm. The wire is in a uniform magnetic field of 0.05 T directed 20° from the vertical, as shown. If a 350 mA current flows clockwise in the wire, find the magnetic force on the wire.
- 20. A circular current loop of radius 18 cm has 250 turns of wire and carries a current of 25 mA. It is placed in a magnetic field of 0.06 T. Find the magnitude of the torque on the loop. Which way will the loop turn?

ANSWERS: (1) 72 μ C (2) 1.13 x 10² m² (3) 1.2 x 10⁴ V/m

(4)
$$Q_1$$
: 16 μ C, 8 V; Q_2 : 12 μ C, 4 V; Q_3 : 4 μ C, 4 V

(5) C_1 : 6.4 x 10⁻⁵ J; C_2 : 2.4 x 10⁻⁵ J; C_3 : 8 x 10⁻⁶ J

(6) 0.4 Ω (7) 2 A (8) 2 V (9) 0.75 W (10) 30 V

(11)
$$i_1 + i_2 = i_3$$
; $\mathcal{E}_1 - i_1 R_1 - \mathcal{E}_2 + i_2 R_2 - i_1 R_4 = 0$;

 \mathcal{E}_2 - $i_3 R_3$ - $i_2 R_2$ = 0 (12) 0.1 s (13) 2.88 x 10⁻² s; 150 µC

(14) 1.5 x 10^{-3} A; 5.52 x 10^{-4} A (15) 4.32 x 10^{-13} N

(16) 1.31 x 10^{-5} s (17) 3.93 x 10^{12} m/s²; 5.09 cm

- (18) 6.75 x 10^{-2} N, out of page (19) 1.57 x 10^{-3} N, out of page
- (20) 2.45 x 10^{-2} N^{.m}, clockwise





