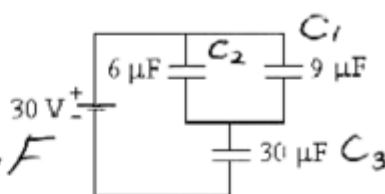


Name: KEY

PHYSICS 2220 - EXAM #2 - SPRING 2009

1. a. Find the equivalent capacitance and the charge on the $9 \mu\text{F}$ capacitor.



$$C_{12} = C_1 + C_2 = 9 \mu\text{F} + 6 \mu\text{F} = 15 \mu\text{F}$$

$$C_{eq} = \frac{C_{12} C_3}{C_{12} + C_3} = \frac{(15 \mu\text{F})(30 \mu\text{F})}{15 \mu\text{F} + 30 \mu\text{F}} = \boxed{10 \mu\text{F}}$$

The charge on each series capacitor (C_{12} and C_3) is

$$Q_{12} = Q_3 = C_{eq} V = (10 \mu\text{F})(30 \text{V}) = 300 \mu\text{C}$$


So

$$Q_1 + Q_2 = 300 \mu\text{C} \text{ and } V_1 = V_2 \Rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$\Rightarrow Q_2 = Q_1 \frac{C_2}{C_1} = Q_1 \frac{6 \mu\text{F}}{9 \mu\text{F}} = \frac{2}{3} Q_1$$

$$\Rightarrow Q_1 + \frac{2}{3} Q_1 = 300 \mu\text{C} \Rightarrow \frac{5}{3} Q_1 = 300 \mu\text{C} \Rightarrow \boxed{Q_1 = 180 \mu\text{C}}$$

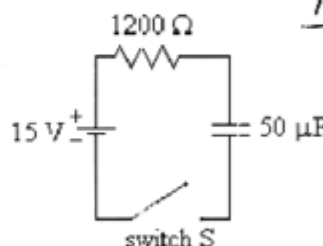- b. The switch S is closed at $t = 0$. Find the energy stored by the capacitor when $t = 3.5 \times 10^{-2} \text{ s}$.



$$q = q_0 (1 - e^{-t/RC})$$

$$\text{with } q_0 = CV = 50 \mu\text{F}(15 \text{V}) = 750 \mu\text{C}$$


$$\text{So } q = 750 \mu\text{C} (1 - e^{-(3.5 \times 10^{-2} \text{ sec}) / (1200 \Omega)(50 \times 10^{-6} \text{ F})})$$

$$\approx 331.5 \mu\text{C}$$

$$\text{Thus } U = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \frac{(331.5 \times 10^{-6} \text{ C})^2}{50 \times 10^{-6} \text{ F}}$$

$$= \boxed{1.10 \times 10^{-3} \text{ J}}$$

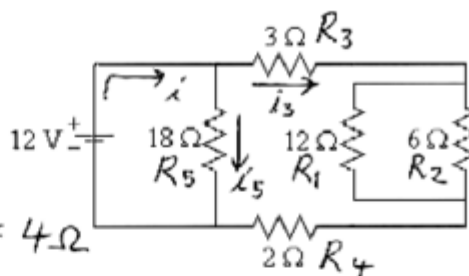2. a. Find the equivalent resistance and the power dissipated by the $3\ \Omega$ resistor.



$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(12\ \Omega)(6\ \Omega)}{12\ \Omega + 6\ \Omega} = 4\ \Omega$$

$$R_{1234} = R_{12} + R_3 + R_4 = 4\ \Omega + 3\ \Omega + 2\ \Omega = 9\ \Omega$$


$$R_{eq} = \frac{R_{1234} R_5}{R_{1234} + R_5} = \frac{9\ \Omega (18\ \Omega)}{9\ \Omega + 18\ \Omega} = \boxed{6\ \Omega}$$

$$i = \frac{V}{R_{eq}} = \frac{12\text{V}}{6\ \Omega} = 2\text{A} \text{ and } i_5 = \frac{12\text{V}}{18\ \Omega} = \frac{2}{3}\text{A}$$

$$\text{So } i_3 = i - i_5 = 2\text{A} - \frac{2}{3}\text{A} = \frac{4}{3}\text{A}$$

$$\text{Thrs } P_3 = i_3^2 R_3 = \left(\frac{4}{3}\text{A}\right)^2 (3\ \Omega) = \boxed{5.33\text{ W}}$$

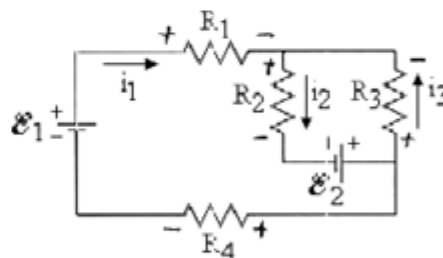
- b. Use Kirchhoff's rules to write down three equations that can be solved for the currents i_1 , i_2 , and i_3 . You do not have to solve the equations! (If you use another system, label your current loops and clearly explain how the values of i_1 , i_2 , and i_3 are related to your currents.)



$$i_1 + i_3 = i_2$$

$$\left. \begin{aligned} E_1 - i_1 R_1 - i_2 R_2 + E_2 - i_1 R_4 &= 0 \\ E_1 - i_1 R_1 + i_3 R_3 - i_1 R_4 &= 0 \\ E_2 - i_3 R_3 - i_2 R_2 &= 0 \end{aligned} \right\} \text{any two}$$

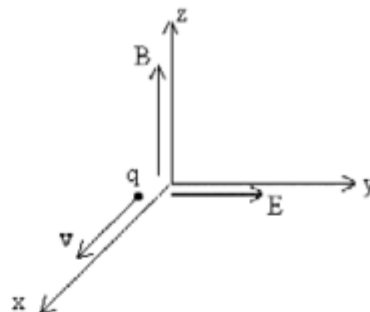3. In a laboratory, there is a uniform electric field of 3000 N/C in the positive y-direction, and a uniform magnetic field of 0.12 T in the positive z-direction. A positively charged particle travels in the positive x-direction (out of the page).




- a. If the electric and magnetic forces on the particle cancel so there is no net force, find the speed of the particle.

$$qvB \sin \phi = qE \quad \text{with } \phi = 90^\circ$$

$$vB = E$$

$$v = \frac{E}{B} = \frac{3000 \frac{\text{N}}{\text{C}}}{0.12 \text{ T}} = \boxed{2.5 \times 10^4 \frac{\text{m}}{\text{sec}}}$$

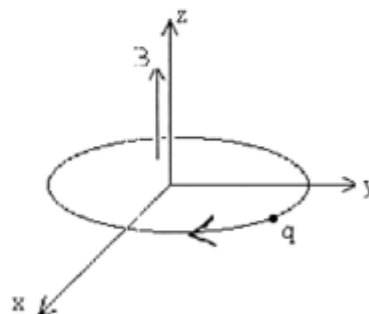- b. If the electric field is suddenly turned off, the positively charged particle moves in a circle of radius 4.35 millimeters in the x-y plane. If the particle's mass is $6.68 \times 10^{-27} \text{ kg}$, find the charge of the particle. Draw the direction of the particle's motion on the diagram.



$$r = \frac{mv}{qB}$$

$$\text{so } q = \frac{mv}{rB} = \frac{(6.68 \times 10^{-27} \text{ kg})(2.5 \times 10^4 \frac{\text{m}}{\text{sec}})}{(4.35 \times 10^{-3} \text{ m})(0.12 \text{ T})}$$

$$\boxed{q = 3.20 \times 10^{-19} \text{ C}}$$