

Homework #5

(27-1) a) For steady current,  $i = \frac{\Delta q}{\Delta t}$ , so

$$\Delta q = i \Delta t = (5.0 \text{ A})(4 \text{ min}) \left( \frac{60 \text{ sec}}{1 \text{ min}} \right) = \boxed{1200 \text{ C}}$$

$$b) \# \text{ electrons} = \frac{\Delta q}{e} = \frac{1200 \text{ C}}{1.6 \times 10^{-19} \text{ C/electron}} = \boxed{7.5 \times 10^{21} \text{ electrons}}$$

(27-2) For a uniform current,  $i = JA = J(\pi r^2) = J(\pi \frac{d^2}{4})$   
where  $d$  = wire diameter. So

$$d = \sqrt{\frac{4i}{J\pi}} = \sqrt{\frac{4(0.5 \text{ A})}{(440 \text{ A/cm}^2) \left( \frac{100 \text{ cm}}{1 \text{ m}} \right)^2 \pi}} = \boxed{3.80 \times 10^{-4} \text{ m}}$$

(27-3) a)  $i = \frac{V}{R} = \frac{23 \text{ V}}{15 \times 10^{-3}} = \boxed{1530 \text{ A}}$  (a huge current!)

$$b) J = \frac{i}{a} = \frac{i}{\pi r^2} = \frac{1530 \text{ A}}{\pi (3 \times 10^{-3} \text{ m})^2} = \boxed{5.41 \times 10^7 \frac{\text{A}}{\text{m}^2}}$$

$$c) R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} \text{ so } \rho = \frac{\pi r^2 R}{L}$$

$$\rho = \frac{\pi (3 \times 10^{-3} \text{ m})^2 (15 \times 10^{-3} \Omega)}{4 \text{ m}} = 1.06 \times 10^{-7} \Omega \cdot \text{m}$$

From Table 27.1, the wire is made of platinum

(27-4) a)  $J = \sigma E$  and  $J = (n_+ + n_-)e n_d$

(Note That the motion of both the positive and negative ions count as positive current flow, since they are in opposite directions)

$$\sigma E = (n_+ + n_-)e n_d$$

$$n_d = \frac{\sigma E}{(n_+ + n_-)e}$$

$$= \frac{(2.7 \times 10^{-14} \Omega \cdot \text{m})(120 \text{ V/m})}{(620 \text{ /cm}^3 + 550 \text{ /cm}^3) \left( \frac{100 \text{ cm}}{1 \text{ m}} \right)^3 (1.6 \times 10^{-19} \text{ C})}$$

$$\boxed{v_d = 1.73 \times 10^{-2} \text{ m/sec}}$$

$$b) J = \sigma E = (2.7 \times 10^{-14} \frac{1}{\Omega \cdot m}) (120 \frac{V}{m}) = \boxed{3.24 \times 10^{-12} \frac{A}{m^2}}$$

(27-5) Using  $P = iV$ ,

$$\Delta q = i \Delta t = \frac{P}{V} \Delta t = \left( \frac{7 \text{ W}}{9 \text{ V}} \right) (5 \text{ hr}) \left( \frac{3600 \text{ sec}}{1 \text{ hr}} \right) = \boxed{1.40 \times 10^4 \text{ C}}$$


$$(27-6) a) \# \text{ electrons} = \frac{\Delta q}{e} = \frac{i \Delta t}{e} = \frac{(0.5 \text{ A})(0.1 \times 10^{-6} \text{ sec})}{1.6 \times 10^{-19} \text{ C/electron}}$$

$$= \boxed{3.13 \times 10^{11} \text{ electrons}}$$

$$b) \text{ ave } i_{\text{ave}} = \frac{\Delta q}{\Delta t} = \frac{(500)(0.5 \text{ A})(0.1 \times 10^{-6} \text{ sec})}{1 \text{ sec}} = \boxed{2.5 \times 10^{-5} \text{ A}}$$

$$c) \text{ peak power } P = iV = (0.5 \text{ A})(50 \times 10^6 \text{ V}) = \boxed{2.5 \times 10^7 \text{ W}}$$
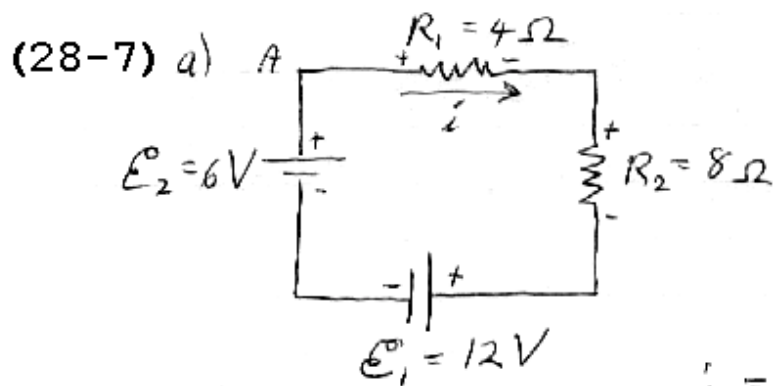
$$\text{ave power } P_{\text{ave}} = i_{\text{ave}} V = (2.5 \times 10^{-5} \text{ A})(50 \times 10^6 \text{ V}) = \boxed{1250 \text{ W}}$$



Going clockwise from A,

$$-iR_1 - iR_2 - E_1 + E_2 = 0$$

$$-i(R_1 + R_2) = E_1 - E_2$$

$$i = \frac{-(E_1 - E_2)}{R_1 + R_2} = \frac{-(12 \text{ V} - 6 \text{ V})}{4 \Omega + 8 \Omega} = \boxed{-0.5 \text{ A}}$$

The current goes the other way counterclockwise


$$b) P_1 = i^2 R_1 = (0.5 \text{ A})^2 (4 \Omega) = \boxed{1.0 \text{ W}}$$

$$P_2 = i^2 R_2 = (0.5 \text{ A})^2 (8 \Omega) = \boxed{2.0 \text{ W}}$$

c) Battery 1 is discharging:  $P = iV = (0.5 A)(12 V) = \boxed{6.0 W}$

Battery 2 is charging:  $P = iV = (0.5 A)(6 V) = \boxed{3.0 W}$

(28-8)

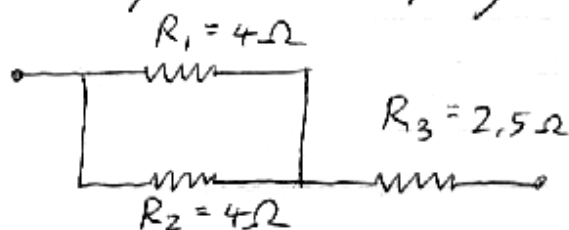

$R_1$  and  $R_2$  are in parallel,

so  $R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(4 \Omega)(4 \Omega)}{4 \Omega + 4 \Omega}$

$$R_{12} = 2 \Omega$$

$R_{12}$  and  $R_3$  are in series, so  $R_{123} = R_{12} + R_3$

$$= 2 \Omega + 2.5 \Omega$$

$$= \boxed{4.5 \Omega}$$


(28-9) There are  $\mathcal{E} = 12 V$  across the  $3 \Omega$  and  $5 \Omega$  resistors, which are in series. The current through these resistors is therefore

$$i = \frac{\mathcal{E}}{3 \Omega + 5 \Omega} = \frac{12 V}{3 \Omega + 5 \Omega} = 1.5 A$$

The voltage across the  $5 \Omega$  resistor is therefore

$$V_{5 \Omega} = iR = (1.5 A)(5 \Omega) = \boxed{7.5 V}$$

(28-10)

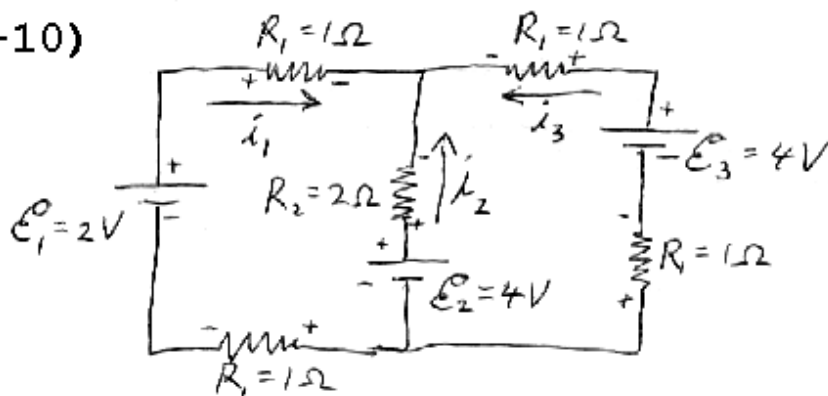

At the top center junction,

$$\boxed{i_1 + i_2 + i_3 = 0}$$

current in = current out

For the left loop, going around clockwise,

$$\boxed{-i_1 R_1 + i_2 R_2 - \mathcal{E}_2 - i_1 R_1 + \mathcal{E}_1 = 0}$$

For the right loop, going around clockwise,

$$\boxed{i_3 R_1 - \mathcal{E}_3 + i_3 R_1 + \mathcal{E}_2 - i_2 R_2 = 0}$$

Plugging in values for the resistors, the boxed equations above are

$$-i_1(2\Omega) + i_2(2\Omega) = -\mathcal{E}_1 + \mathcal{E}_2 = -2V + 4V = 2V$$

$$\boxed{-i_1(2\Omega) + i_2(2\Omega) = 2V} \quad *$$

$$i_3(2\Omega) - i_2(2\Omega) = \mathcal{E}_3 - \mathcal{E}_2 = 4V - 4V = 0$$

$$\boxed{i_3(2\Omega) - i_2(2\Omega) = 0} \quad **$$

And we still have  $\boxed{i_1 + i_2 + i_3 = 0} \quad ***$

Solve equation \*\*\* for  $i_3$ , and substitute into \*\*

$$i_3 = -(i_1 + i_2) \text{ so } -(i_1 + i_2)(2\Omega) - i_2(2\Omega) = 0$$

$$\Rightarrow -(i_1 + i_2) - i_2 = 0 \quad (\text{cancel the } 2\Omega)$$

$$i_1 = -2i_2$$

Now plug this into \*:


$$-(-2i_2)(2\Omega) + i_2(2\Omega) = 2V$$

$$i_2(6\Omega) = 2V \Rightarrow \boxed{i_2 = \frac{1}{3} A}$$

$$\text{Then } i_1 = -2i_2 = -2\left(\frac{1}{3}A\right) = \boxed{-\frac{2}{3}A}$$

( $i_1$  is really going counterclockwise)

$$\text{Finally, } i_3 = -(i_1 + i_2) = -\left(-\frac{2}{3}A + \frac{1}{3}A\right) = \boxed{\frac{1}{3}A}$$

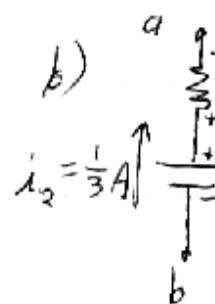b)   $R_2 = 2\Omega$   $V_a - V_b = +E_2 - i_2 R_2$   
 $i_2 = \frac{1}{3}A$   $E_2 = 4V$  (start at b)  $= 4V - \left(\frac{1}{3}A\right)(2\Omega) = \boxed{3\frac{1}{3}V}$

(28-11) a)  $\tau = RC = (1.4 \times 10^6 \Omega)(1.8 \times 10^{-6} F) = \boxed{2.52 \text{ sec}}$

b)  $q_0 = EC = (12V)(1.8 \times 10^{-6} F) = \boxed{2.16 \times 10^{-5} C}$

c)  $q = q_0(1 - e^{-t/RC}) \Rightarrow 1 - \frac{q}{q_0} = e^{-t/RC}$

So  $\ln\left(\frac{q_0 - q}{q_0}\right) = -\frac{t}{RC}$

Using  $-\ln x = \ln \frac{1}{x}$ , this is

$$\frac{t}{RC} = \ln\left(\frac{q_0}{q_0 - q}\right)$$

$$t = \overset{\tau}{RC} \ln\left(\frac{q_0}{q_0 - q}\right) = (2.52 \text{ sec}) \ln\left(\frac{21.6 \mu C}{21.6 \mu C - 16 \mu C}\right) = \boxed{3.40 \text{ sec}}$$

(28-12) a)  $q = q_0 e^{-t/\tau}$  and  $V = \frac{q}{C}$ , so dividing by C

$$\Rightarrow V = V_0 e^{-t/\tau}$$

$$\frac{V}{V_0} = e^{-t/\tau}$$

$$\ln\left(\frac{V}{V_0}\right) = -\frac{t}{\tau}$$

$$\tau = \frac{t}{\ln(V_0/V)} = \frac{10 \text{ sec}}{\ln(100\text{V}/1\text{V})} = \boxed{2.17 \text{ sec}}$$

$$b) V = V_0 e^{-t/\tau}$$

$$= 100 \text{ V } e^{-17 \text{ sec} / 2.17 \text{ sec}}$$

$$= \boxed{3.96 \times 10^{-2} \text{ V}}$$